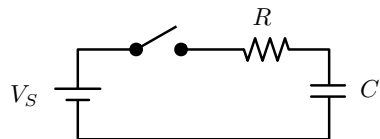
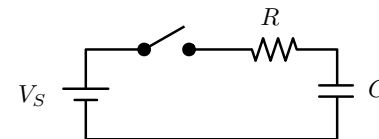


A circuit is built of a battery, a switch, a resistor and a capacitor as shown:  $R = 1.5\text{k}\Omega$ ,  $C = 20\mu\text{F}$  and  $V_S = 10\text{V}$ .



The voltage on the capacitor is 2.0 V before the switch is closed. At time  $t = 0$  switch is closed, this connects the positive terminal of the battery to the resistor. When does the voltage on the capacitor reach 7 volts?

A circuit is built of a battery, a switch, a resistor and a capacitor as shown:  $R = 1.5\text{k}\Omega$ ,  $C = 20\mu\text{F}$  and  $V_S = 10\text{V}$ .



The voltage on the capacitor is 2.0 V before the switch is closed. At time  $t = 0$  switch is closed, this connects the positive terminal of the battery to the resistor. When does the voltage on the capacitor reach 7 volts?

Solution: We can compute the constant

$$\begin{aligned}RC &= (1.5 \times 10^3 \Omega)(20 \times 10^{-6} \text{F}) \\ &= 30 \times 10^{-3} \Omega \cdot \text{F} \\ &= 30 \times 10^{-3} \frac{\text{V}}{\text{A}} \cdot \frac{\text{C}}{\text{V}} \\ &= 30 \times 10^{-3} \frac{\text{C}}{\text{A}} \\ &= 30 \times 10^{-3} \frac{\text{C}}{\text{C/s}} \\ &= 30 \times 10^{-3} \text{s} \\ &= 30 \text{ms}\end{aligned}$$

Now we can use the theorem for the an RC circuit.

$$\begin{aligned}V_C(t) - V_S &= (V_C(0) - V_S) e^{-t/RC} \\ (7\text{V}) - (10\text{V}) &= ((2\text{V}) - (10\text{V})) e^{-t/RC} \\ -3\text{V} &= -8\text{V} e^{-t/RC} \\ \frac{3}{8} &= e^{-t/RC} \\ \ln\left(\frac{3}{8}\right) &= -t/RC \\ t &= -RC \ln\left(\frac{3}{8}\right) \\ t &= -(30\text{ms}) \ln\left(\frac{3}{8}\right) \\ t &= 29.42\text{ms}\end{aligned}$$